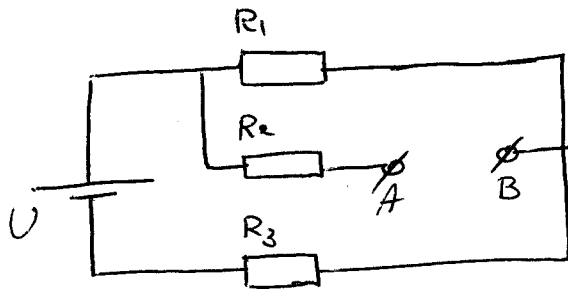


# Thévenin & Norton.

1) Gege:



$$U = 24V$$

$$R_1 = 100\Omega$$

$$R_2 = 20\Omega$$

$$R_3 = 300\Omega$$

Lev:

$V_{AB}$  met  $R_{AB} = 200\Omega$ , gebruik Thévenin

Opv:


A: Open klemspanning  $V_{AB}$ :

$R_2$  wordt niet door stroom doorlopen  $\rightarrow V_{AB} = U_{R_1} = U_{th}$

$$\Rightarrow U_{R_1} = I \cdot R_1 \quad \text{en} \quad I = \frac{U}{R_1 + R_3}$$


$$\begin{aligned} \Rightarrow \text{combineren: } U_{R_1} &= \frac{U}{R_1 + R_3} \cdot R_1 \\ &= \frac{24}{100 + 300} \cdot 100 \\ &= \underline{\underline{6V}} = U_{th} \end{aligned}$$

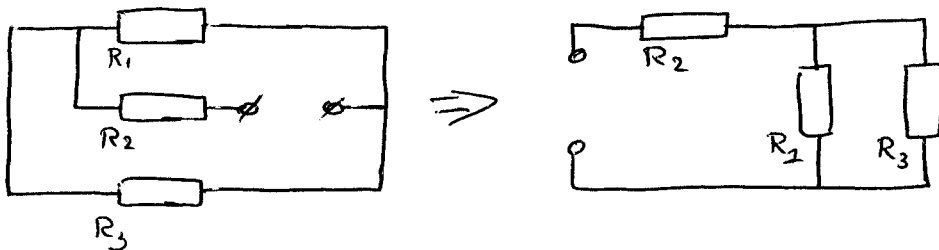B:  $R_{th}$ : bron vervangen door kortsluiting, kijken vanuit A-B:



$$R_{th} = R_2 + \frac{R_2 \cdot R_3}{R_1 + R_3} = 20 + \frac{100 \cdot 300}{100 + 300} = 20 + 75 = 95\Omega$$

C: Vervangingschema:

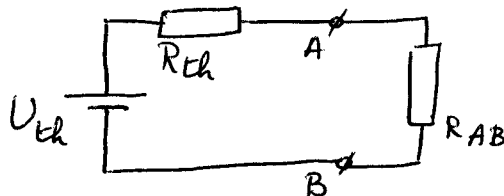

$$\begin{aligned} V_{AB} &= U_{th} \cdot \frac{R_{AB}}{R_{th} + R_{AB}} \\ &= 6 \cdot \frac{200}{95 + 200} \\ &= \underline{\underline{4,0678V}} \end{aligned}$$


# Thévenin & Norton

2) Seq: zie opgave 1

Gev:  $U_{AB}$  met  $R_{AB} = 200 \Omega$ .

Op1:

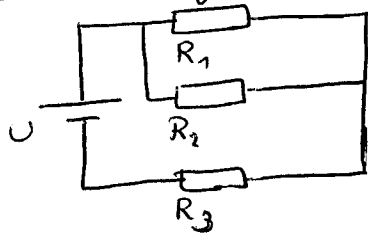A: Verbinding A-B kortsluiten;  $I_{R_2} = I_N$



$$R_T = (R_1 // R_2) + R_3$$

$$= \frac{100 \cdot 20}{100 + 20} + 300$$

$$= 16,66 + 300 = 316,66 \Omega$$

$$I = \frac{U}{R_T} = \frac{24}{316,66} = 0,07579 \text{ A}$$

$$U_{R_2} = U - I \cdot R_3$$

$$= 24 - 0,07579 \cdot 300$$

$$= 24 - 22,737$$


$$= 1,2632 \text{ V}$$

$$I_N = \frac{U_{R_2}}{R_2} = \frac{1,2632}{20} = 0,06316 \text{ A} = \underline{\underline{63,16 \text{ mA}}}$$

B:  $R_N$  berekenen door bron te vervangen door een verbinding:  
(zelfde berekening als oef. 1)

$$\Rightarrow R_{th} = \underline{\underline{95 \Omega}} = R_N$$


C: Nortonschema:

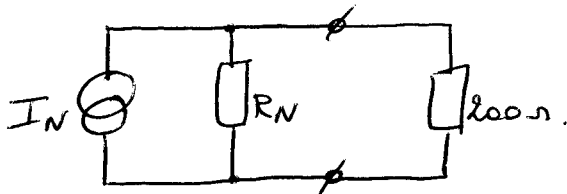

$$U_{AB} = I \cdot \frac{R_N \cdot R_{AB}}{R_N + R_{AB}} = 0,06316 \cdot \frac{95 \cdot 200}{95 + 200} = \underline{\underline{4,0678 \text{ V}}}$$

# Thévenin & Norton

3) Ex:

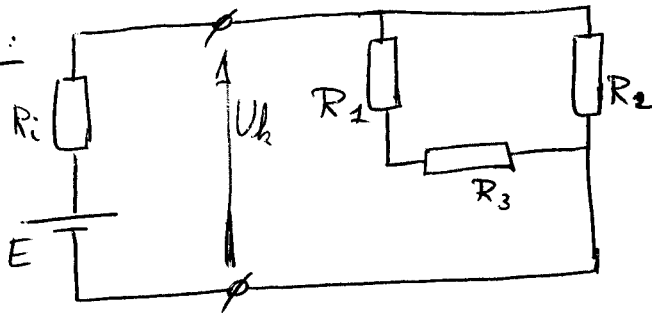

$$E = 12V$$

$$R_i = 2\Omega$$

$$R_1 = 7\Omega$$

$$R_2 = 9\Omega$$

$$R_3 = 11\Omega$$

Gen:  $U_h$  ou  $R_{th}$

Qpl:  
A:  $U_h$

$$R_t = R_i + \left[ (R_1 + R_3) \parallel R_2 \right]$$

$$= 2 + \left[ (7 + 11) \parallel 9 \right]$$

$$= 2 + \left[ 18 \parallel 9 \right]$$

$$= 2 + 6$$

$$= 8\Omega$$


$$I = \frac{E}{R_t} = \frac{12}{8} = 1,5A$$

$$U_h = E - I \cdot R_i$$

$$= 12 - 1,5 \cdot 2$$

$$= \underline{\underline{9V}} = U_h$$

B:  $R_{th}$

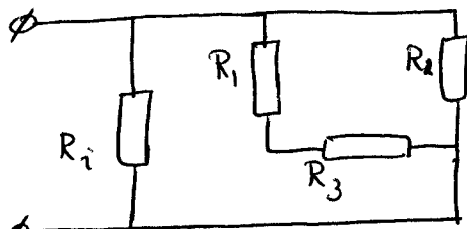


$$R_{th} = R_i \parallel \left[ (R_1 + R_3) \parallel R_2 \right]$$

$$= 2 \parallel 6$$

$$= \underline{\underline{1,5\Omega}} = R_{th}$$

# Thévenin & Norton

4) Geg:

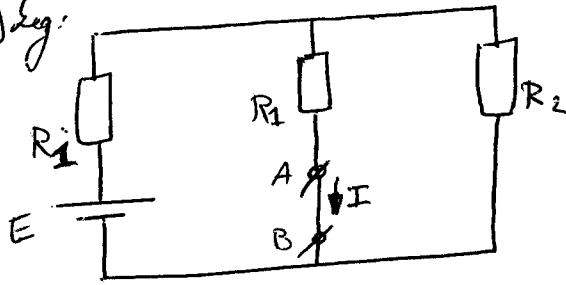

$$E = 12V$$

$$R_i = 2\Omega$$

$$R_1 = 7\Omega$$

$$R_2 = 9\Omega$$

Ges:  $I_{R_2}$

Op1: met Thévenin.


A: Open klemspanning  $U_{AB}$ ,  $R_1$  wordt niet door stroom doorlopen.

$$U_{AB} = E \cdot \frac{R_2}{R_i + R_2} = 12 \cdot \frac{9}{2 + 9} = 9,81818V$$

B:  $R_{th} \Rightarrow E$  vervangen door een verbinding

$$\begin{aligned} R_{th} &= R_1 + (R_2 // R_i) \\ &= 7 + \left( \frac{9 \cdot 2}{9 + 2} \right) \\ &= 7 + 1,63636 \\ &= 8,6364\Omega \end{aligned}$$

C: Schema:

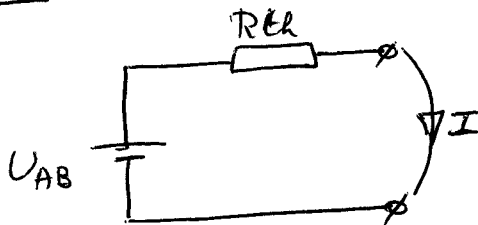

$$\begin{aligned} I &= \frac{U_{AB}}{R_{th}} \\ &= \frac{9,81818}{8,6364} \\ &= \underline{\underline{1,13684A}} \end{aligned}$$